

## (92) MAGNITUDE & TIME SCALING TECHNIQUES

- In the process of solving the problems no consideration has so far been given to the magnitudes of the problem - variables or the time required for solving each problem.
- Equipment constraints usually restrict the maximum voltage output of each ~~amp~~ amplifier (to 10 volts).
- Thus, amplifier overload would occur when the problem dictates a large voltage output — thus, the problem must be magnitude scaled to fit the computer range.
- It would be necessary to scale up some parts of a problem & scale down other parts.
- For example: if the problem of calculating rocket speed is solved then it would be impossible to relate 1 volt on computer to 1 ft/sec in real problem. However, it may be solved by relating 1 volt on computer to 1 mile/sec in real problem — by magnitude scaling up.
  - Again, in the same problem an acceleration term might have a maximum value of  $1 \text{ ft/sec}^2$  — which on basic unit of mile for length would give a voltage of approximately 0.002 volt — which is in the noise level of signal & would yield erroneous results. — so it would be required to be scaled-up.
- # Thus, one basic change of units for the entire problem may not work.
- Time scaling is needed when one intends to study a physical phenomenon that ~~also~~ evolves much faster or slower than is convenient for the computer operator.
  - For example: If one wishes to study planetary motion then he may not have the time to wait for a complete period of revolution about the sun — in fact an actual time of one year may be represented as 10 seconds (say) of computer time.





## ⑧ Magnitude Scaling - Basic Principles:

■ Consider the differential equation:  $\frac{dx}{dt} + 0.1x = 5; x(0) = 0$

• Analytical Solution:

$$x(t) = 50(1 - e^{-0.1t})$$

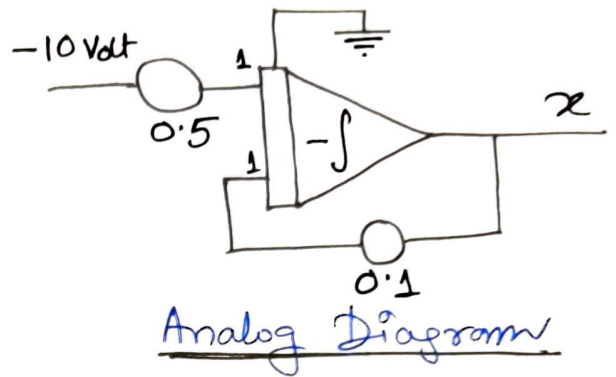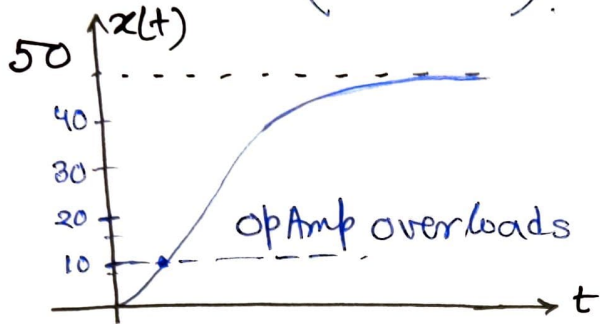

- The amplifier overloads — as it cannot supply 50 volts.
- To avoid this difficulty a different correspondence must be set up between the problem variable ( $x$ ) & computer voltage  $e$ .
- Since, maximum value of  $V$  is 10 volt, let 5 units of  $x$  to correspond to 1 volt of  $V$ , i.e.,  $V = x/5$  — thus, amplifier won't be overloaded.
- The analogous equation is:  $\frac{dV}{dt} + 0.1V = 1$  &  $V(0) = 0$   
 & the analytic solution is:  $V(t) = 10(1 - e^{-0.1t})$

■ The basic idea is that the analog simulation does not solve the actual equation but an analogous equation.

■ Analog voltages normalized to units — it is common practice to redefine the magnitudes of reference voltages & all associated input & output voltages on an analog computer in terms of a quantity called the "Analog Unit" (or "Unit").

- By definition the maximum voltage obtainable on the computer is one unit — thus for a  $\pm 10$  volt computer, 1 unit = 10 volts
- Scaling problems in terms of units makes the scaled analog diagram machine-independent, i.e., good for 100 volt as well as 10 volt machines.

## 94) A systematic approach to Magnitude Scaling

— Objective: To construct a scaled analog diagram for  $\frac{dx}{dt} + 0.1x = 5, x(0) = 0$  so that the maximum range of the amplifier is utilized but will not cause any overload.

▣ Step 1: Draw the unscaled analog diagram. Note that +10 volt is assumed to be the maximum reference voltage available on the computer.

▣ Step 2: Estimate the maximum value of each variable appearing as an amplifier output only (since all other elements have a gain less than unity — their output need not be considered).

In present case  $x(t)$  is the only amplifier output which has a maximum value of 50.

▣ Step 3: Define a scaling relationship between each problem variable & the corresponding computer variable.

In present case,  $|x|_{\max} = 50$ , which may be represented as a voltage  $V_x$  on the analog computer.

Now,  $V_x$  can vary from -10 volt to 0 volt to +10 volt, whereas  $x$  can vary from 0 to 50. Therefore, +10 volt would represent 50.

• Thus, one may write,  $V_x = \frac{x}{5} = L_x x$ , with,  $L_x$ : level of  $x = \frac{1}{5}$

• In general, one may choose,  $L_x = \frac{10}{|x|_{\max}}$

• For any variable having variation from -100 to 100, one may use  $L_x = \frac{1}{10}$  & +10 & -10 volt would represent 100 & -100, respectively.

• Scaling Table:

Problem Variable	Estimated Maximum	Level	Computer Variable	I.C.	Scaled I.C.
$x$	50	$\frac{1}{5}$	$[x/5]$	0	$[0]$

▣ Step 4: Write down the scaled analog equations for each amplifier in terms of the computer variables (amplifier outputs) defined in step 3. No other variable should appear in these equations.



- For the present example, solving for the derivative, one can write,  $\frac{dx}{dt} = 5 - 0.1x$ ,  $x(0) = 0$ .

- To get this equation in terms of the computer variable, divide/multiply each term by  $Lx = 1/5$  to get,

$$\frac{d}{dt} \left( \frac{5x}{5} \right) = 5 - 0.1 \left( \frac{5x}{5} \right), \quad x(0) = 0$$

- Now, regrouping the constants, so that all variables are computer variables, one gets,

$$5 \cdot \frac{d}{dt} \left[ \frac{x}{5} \right] = 5 - 0.5 \left[ \frac{x}{5} \right], \quad \left[ \frac{x}{5} \right](0) = 0.$$

$$\text{or, } \underline{\underline{\frac{d}{dt} \left[ \frac{x}{5} \right] = 1 - 0.1 \left[ \frac{x}{5} \right]}}, \quad \underline{\underline{\left[ \frac{x}{5} \right](0) = 0}}$$

Step 5: Draw the scaled analog diagram using equations obtained in step 4. & label all the computer variables on the diagram.

- The scaled diagram is of the same form as the original one, but will have different pot values & amplifier gains.


- The output of the analog diagram shows the response of  $\left[ \frac{x}{5} \right]$ , i.e., the analog variable in volts.

- To find actual value of  $x$  (say at time  $t_1$ ) one needs to use the value of  $Lx$ .


- Thus, actual value of  $x$  at  $t = t_1$ ,  $5 \times 5 = 25$ .

Note: Constants are realized by patching a  $\pm 10$  volt reference to some pot set at a particular value. To be consistent with the magnitude scaling method the pot setting must be found using some formula.

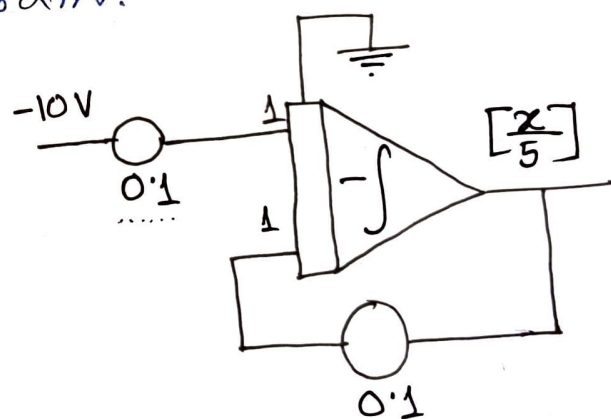- Initial condition, is the value of variable at  $t=0$ , & it should be similarly scaled to obtain the exact value of pot setting - a consideration on  $\pm 10$  volt voltage level.



Scaled Diagram

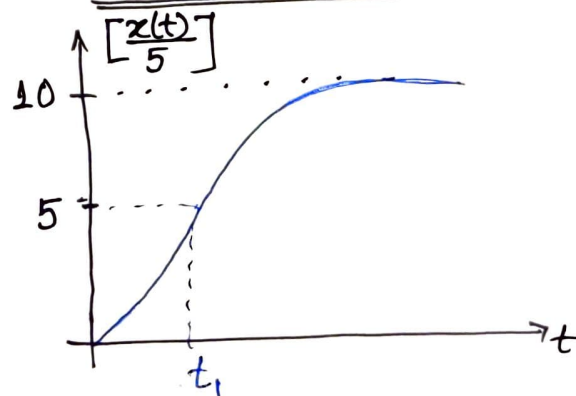


Time response



96) Example: Magnitude-scale the following problem so that no over-load occurs & maximum range is used.

$$\frac{d^2x}{dt^2} + 2\frac{dx}{dt} + 25x = 0; \quad x(0) = 20; \quad \dot{x}(0) = 0; \quad |x| \leq 20 \text{ \& } |\dot{x}| \leq 100.$$

- Solving for  $\ddot{x}$ , one gets,  $\ddot{x} = -25x - 2\dot{x}$
- The level constants are:  $L_x = \frac{10}{20} = \frac{1}{2}$  &  $L_{\dot{x}} = \frac{10}{100} = \frac{1}{10}$ .
- Thus, from the given problem,  $\ddot{x} = -25 \times 2 \left[ \frac{x}{2} \right] - 2 \times 10 \left[ \frac{\dot{x}}{10} \right]$ , with,  $\left[ \frac{x}{2} \right]$  &  $\left[ \frac{\dot{x}}{10} \right]$  are computer variables.
- Similarly for initial conditions,  $\left[ \frac{x}{2} \right](0) = 10$  &  $\left[ \frac{\dot{x}}{10} \right](0) = 0$ .
- In order to get  $-\left[ \dot{x}/10 \right]$  to be the output of an amplifier,  $\left[ \frac{\ddot{x}}{10} \right]$  must be the input to the amplifier (integrator).
- Realizing the above fact, one needs to divide the equation by 10 to get,  $\frac{\ddot{x}}{10} = -5 \left[ \frac{x}{2} \right] - 2 \left[ \frac{\dot{x}}{10} \right]$ .
- The initial condition for amplifier (A) should be grounded to emulate  $\left[ \frac{\dot{x}}{10} \right](0) = 0$  & that of (B) should be connected to a -10Volt to emulate  $\left[ \frac{x}{2} \right](0) = 10$ .

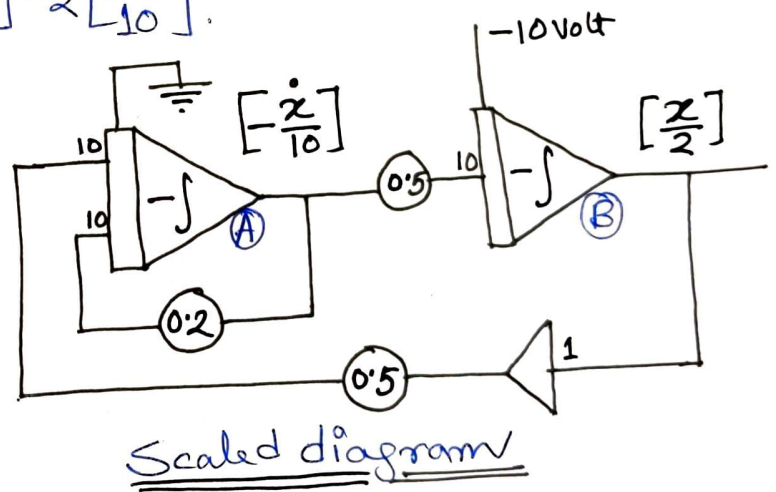

Example: Simulate  $y = ax$ ,  $|x|_{\max} = 20$ ,  $|y|_{\max} = 40$  &  $a = -3$ .


• Let,  $V_x = L_x x$  &  $V_y = L_y y$

• Now,  $V_y = L_y y = -K G V_x = -K G L_x x$

$$\Rightarrow y = \frac{-K G L_x}{L_y} x \Rightarrow a = \frac{-K G L_x}{L_y}, \text{ or } \boxed{K = \frac{-a L_y}{G L_x}}$$

• In our case,  $L_x = \frac{1}{2}$  &  $L_y = \frac{1}{4}$

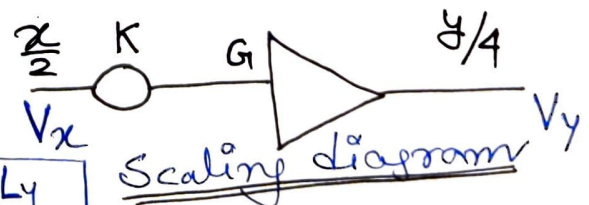• Thus,  $K = \frac{-1/4}{1/2} \cdot \frac{-3}{1} = 1.5/G$



- Level out: level of variable immediately following the pot to be set.
- Level in: level of variable preceding the pot.
- Gain: gain of the amplifier following pot.

$$\# K = \frac{\text{Level out}}{\text{Level in}} \times \frac{|\text{Co-efficient}|}{\text{Gain}}$$

• Co-eff. relates to the equation to